

EECE 5141C/6041C

Introduction to Mechatronics

Lab 3: Switch Debouncing and Edge Counting

Name: _____

In this lab, you will design, program, and construct a simple microcontroller system capable of debouncing a single switch input and counting rising edges.

DELIVERABLES

1. Completed Worksheet
2. Annotated Source Code

SYSTEM DESCRIPTION

The microcontroller must monitor one digital input supplied by the provided spinner assembly. The spinner assembly utilizes a single-pole, double-throw switch. However, this switch can also be used as a single-pole, single-throw switch by connecting only one of the throw terminals. (Note: One throw is normally open, and one throw is normally closed.) In this lab, you will debounce the switch signal and count switch transitions using two methods: one software method and one hardware method. The microcontroller should also display the current number of counted edges in hexadecimal format using two seven-segment displays.

Preliminary Switch Characterization

Construct a pull up switch circuit as shown in Figure 1 using the normally open throw of the spinner switch. Using the oscilloscope, measure the output signal of the circuit as you rotate the spinner and trigger the switch. Sketch the measured signal in Question 1 of the Design Questions Section. Be sure to indicate the approximate settle time as well as the approximate pulse length of the bouncing signals. Using these measurements, determine the amount of time your software should measure a constant signal before declaring the switch settled and answer Question 2.

 


Figure 1: Pull-Up Switch Circuit

Method 0: No Debouncing

In order to demonstrate the need for switch debouncing, we will first implement a simple edge counting algorithm that only looks for pin transitions without any debouncing. This can be accomplished with a simple modification of your code from Lab 2. The first modification requires the addition of edge detection logic within the main `while(1)` loop. This is accomplished by comparing the previous pin value with the current pin value for each iteration of the `while(1)` loop. Each time there is a 1 to 0 transition, a falling edge has occurred and an `edge_count` variable should be incremented. Now, instead of displaying the value of the 8 input switches from the previous lab (which we are no longer using), we will display the current value of an `edge_count`. Once implemented, slowly rotate the spinner to trigger the switch. Record your observations in Question 3.



Method 1: Software Debounce and Software Edge Counting

Method 3: Hardware Debounce and Counting via Timer 0 Clock

Figure 3: SR Latch Debounce Circuit

DESIGN QUESTIONS

1. Sketch the measured output signal from your pull-up resistor circuit. Indicate the approximate settle time as well as the approximate pulse length of the bouncing signals.
2. Based on your observations in Question 1, what is a reasonable amount of time to wait until declaring the switch signal stable? Why?
3. When implementing Method 0, record the behavior of the counted value as you slowly rotate the spinner.
4. When implementing a 16-bit long match pattern, what sample rate would your Timer 1 need to generate in order to detect a settled signal based on your answer of Question 2? What Timer 1 clock source and OCR1A values are needed to generate this sample rate.

5. Suppose you needed to observe and debounce 64 input signals. From a system cost perspective (assuming your design and programming time is free), would you implement hardware or software debouncing? Why?
6. Are there any reasons we should not use arbitrarily long match patterns for our shift and match algorithm? For example, we could use 256-bit long patterns. Why might this be a bad idea?
7. Conversely, we could also use 2-bit long patterns (for example 0b10 for falling edge and 0b01 for rising edge). Why might this be a bad idea? Is this similar to any other methods we have discussed?
8. When using a hardware debouncing circuit (such as the SR latch debouncer), you could implement a software edge detector similar to the shift and pattern match method. How long (how many bits) of a pattern should you use? Why? Is this similar to any other methods we discussed?